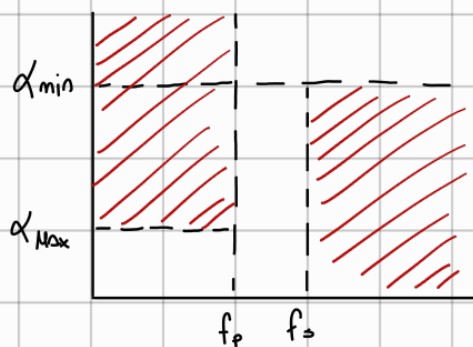


Platillo.



$\alpha_{max} [db]$	ω_p	ω_s
1	1	1,25

1) Queremos un retardo de grupo cte, mismo retardo para todas las frecuencias.

$$D(\omega) = - \frac{\partial \phi(\omega)}{\partial \omega}$$

Aproximación Storch.

$$H(j\omega) \Big|_{\omega=s/j} = e^{-\cancel{j} \frac{st}{\cancel{j}}} = e^{-st}$$

$$H(j\omega) = \frac{P(s)}{Q(s)} = e^{-st} = \frac{1}{\sinh(s) + \cosh(s)}$$

$$\sinh(x) = \frac{e^x - e^{-x}}{2} \quad \cosh(x) = \frac{e^x + e^{-x}}{2}$$

m=1

$$\coth(s) = \frac{1}{s} = \frac{\cosh(s)}{\sinh(s)}$$

$$e^x = \sinh(x) + \cosh(x)$$

$$\sinh(s) = s + \frac{s^3}{3!} + \frac{s^5}{5!} + \frac{s^7}{7!} + \dots$$

$$H(s) = \frac{1}{\sinh(s) + \cosh(s)} = \frac{1}{s+1}$$

$$\cosh(s) = 1 + \frac{s^2}{2!} + \frac{s^4}{4!} + \frac{s^6}{6!} + \dots$$

$$H_{B1}(s) = \frac{1}{s+1}$$

expansión en fracciones continuas

$$\coth(s) = \frac{\cosh(s)}{\sinh(s)} = \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{1}{\frac{5}{s} + \frac{1}{\frac{7}{s} + \frac{1}{\frac{9}{s} + \dots}}}}$$

suponiendo que $D(\omega) = \frac{a_1}{a_0} \left[1 + \left(\frac{1}{a_0} - \frac{a_1^2}{a_0^3} + \frac{2}{a_0} \right) \omega^2 + \dots \right]$

Para $D(0) = \frac{a_1}{a_0} = \frac{1}{1} \rightarrow D(0) = 1$

todos los impares.

m=2

$$\coth(s) = \frac{1}{s} + \frac{s}{3} = \frac{3+s^2}{3s}$$

$$H_{B2}(s) = \frac{3}{s^2 + 3s + 3}$$

$$D(0) = \frac{a_1}{a_0} = \frac{3}{3} \rightarrow D(0) = 1$$

$$m=3$$

$$\text{Cotgh}(s) = \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{s}{5}} = \frac{1}{s} + \frac{5s}{1s + s^2} = \frac{6s^2 + 15}{s^3 + (15)s}$$

$$H_{B3}(s) = \frac{15}{s^3 + 6s^2 + (15)s + 15}$$

$$D(0) = \frac{a_1}{a_0} = \frac{15}{15} \rightarrow D(0) = 1$$

$$m=4$$

$$\text{Cotgh}(s) = \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{1}{\frac{5}{s} + \frac{1}{\frac{7}{s}}}} = \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{1}{\frac{5}{s} + \frac{7}{s^2}}}} = \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{7s}{35 + s^2}}$$

$$\text{Cotgh}(s) = \frac{1}{s} + \frac{1}{\frac{105 + (3)s^2 + 7s^2}{s^3 + (35)s^2}} = \frac{1}{s} + \frac{s^3 + (35)s}{(10)s^2 + (105)} = \frac{s^4 + (45)s^2 + 105}{(10)s^3 + (105)s}$$

$$\text{Cotgh}(s) = \frac{s^4 + (45)s^2 + 105}{(10)s^3 + (105)s}$$

$$H_{B4}(s) = \frac{105}{s^4 + (10)s^3 + (45)s^2 + (105)s + 105}$$

$$D(0) = \frac{a_1}{a_0} = \frac{105}{105}$$

$$D(0) = 1$$

$$2) \alpha = -20 \log(|t(j\omega)|) = 10 \log(|t(j\omega)|^{-2}) = 10 \log\left(\frac{B_n(j\omega)^2}{B_n(0)^2}\right)$$

$$P_{\text{max}} n=2$$

$$t_{B2}(j\omega) = \frac{3}{(j\omega)^2 + (j\omega)(3) + 3} \rightarrow \omega_p = 1 \quad t(j) = \frac{3}{-1 + j3 + 3}$$

$$|t(j)|^2 = \frac{(3)^2}{(2)^2 + (3)^2} \rightarrow \alpha(1\%s) = 10 \log\left(\frac{(2)^2 + (3)^2}{(3)^2}\right) \rightarrow \alpha(1\%s) = 1,59 \rightarrow \alpha_{\text{max}} \quad \text{⊗}$$

$$P_{\text{max}} n=3$$

$$t_{B3}(j\omega) = \frac{15}{(j\omega)^3 + 6(j\omega)^2 + 15(j\omega) + 15} \rightarrow t_{B3}(j) = \frac{15}{-j - 6 + j15 + 15} = \frac{15}{9 + j14}$$

$$|t_{B3}(j)|^2 = \frac{196}{81 + 196} \quad \alpha(1\%s) = 10 \log\left(\frac{277}{225}\right) \rightarrow \alpha(1\%s) = 0,9 \quad \text{Ⓢ}$$

La $T(s)$ que cumple con el α_{max} es la de orden $N=3$

$$T_{B3}(s) = \frac{15}{s^3 + s^2 + 15s + 15}$$

3)

$$D_{B3}(w) = \frac{6w^4 + 45w^2 + 225}{w^6 + 6w^4 + 45w^2 + 225} \rightarrow D_{B3}(z,s) = \frac{6(z,s)^4 + 45(z,s)^2 + 225}{(z,s)^6 + 6(z,s)^4 + 45(z,s)^2 + 225}$$

$$D_{B3}(z,s) = 0,752 \text{ seg.}$$


$$\text{Error} = \frac{D(z,s) - D(\emptyset)}{D(\emptyset)} \quad 100$$

$$\text{Error} = \frac{0,752 - 1}{1} \cdot 100 \Rightarrow$$

$$\text{Error} = -24,8\%$$

4)

topologia Sallen-Key

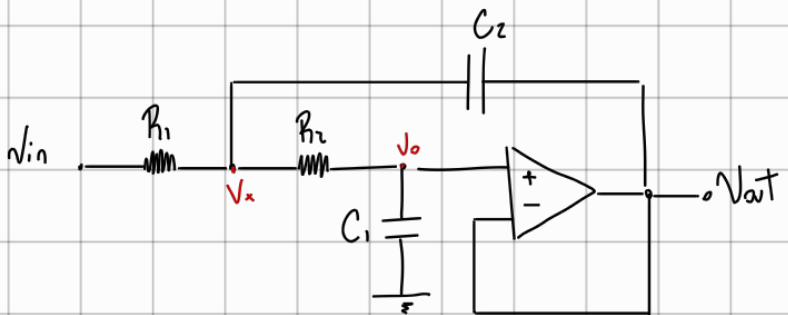

Con $k=1$

$$(1) N_x(G_1 + G_2 + sC_2) = N_o(G_2 + sC_2) + V_i$$

$$(2) N_o = N_x \frac{G_2}{sC_1 + G_2}$$

$$V_o \left[\frac{(sC_1 + G_2)(G_1 + G_2) + s^2 C_1 C_2 + sC_1 G_2 - G_2 - sC_2}{G_2} \right] = N_i G_1$$

$$N_o \left[\frac{sC_1 G_1 + sC_1 G_2 + G_1 G_2 + \cancel{G_2^2} + s^2 C_1 C_2 + sC_1 G_2 - \cancel{G_2^2} - sC_2 G_2}{G_1 G_2} \right] = N_i$$

$$N_o \left[\frac{s^2 C_1 C_2 + sC_1 G_2 + sC_1 G_1 + G_1 G_2}{G_1 G_2} \right] = N_i \rightarrow \frac{N_o}{N_i} = \frac{G_1 G_2}{C_1 C_2} \cdot \frac{1}{s^2 + s \frac{1}{C_2} (G_1 + G_2) + \frac{G_1 G_2}{C_1 C_2}}$$

$$f_{sk}(s) = \frac{V_o(s)}{V_i(s)} = \frac{G_1 G_2}{C_1 C_2} \cdot \frac{1}{s^2 + s \frac{1}{C_2} (G_1 + G_2) + \frac{G_1 G_2}{C_1 C_2}} = \frac{k \cdot \omega_o^2}{s^2 + s \frac{\omega_o}{Q} + \omega_o^2}$$


$$f_{sk}(s) = \frac{\frac{G_1 G_2}{C_1 C_2}}{s^2 + s \frac{1}{C_2} (G_1 + G_2) + \frac{G_1 G_2}{C_1 C_2}}$$

Factorización $H_{B3}(s) = \frac{15}{s^3 + 6s^2 + (15)s + 15} \rightarrow \phi \quad s = -2,322$

-2,322	1	6	15	15
		-2,322	-8,54	-15
	1	3,678	6,46	ϕ

$$H_{B3}(s) = \frac{1}{(s+2,322)} \cdot \frac{15}{(s^2 + s(3,678) + 6,46)}$$

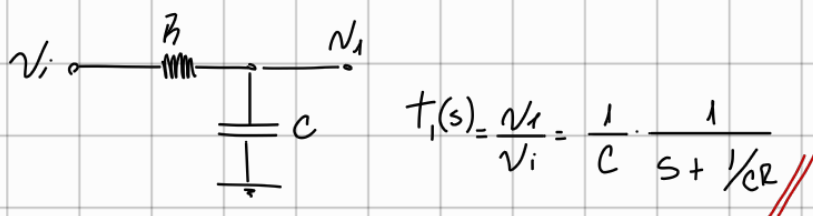El polinomio de Bessel es de orden 3 por lo tanto utilizo dos circuitos en cascena



$$T(s) = T_1(s) \cdot T_{s-k}(s) = \left(\frac{1}{C_3}\right) \left(\frac{1}{s + \frac{1}{C_3 R_3}}\right) \left(\frac{G_1 G_2}{C_1 C_2}\right) \left(\frac{1}{s^2 + s \frac{1}{C_2} (G_1 + G_2) + \frac{G_1 G_2}{C_1 C_2}}\right)$$

Normalización


$$R_3 = 1 \quad \frac{1}{C_3 R_3} = 2,322 \rightarrow C_3 = \frac{1}{(2,322) R_3} \quad G_1 = G_2 = 1 \quad \frac{1}{C_1 C_2} = 6,46$$

$$\frac{\omega_0}{Q} = 3,678 = \frac{1}{C_2} (G_1 + G_2) \quad C_1 = \frac{1}{C_2 (6,46)}$$

$$C_2 = \frac{2 G_1}{3,678}$$

$$G_1 = G_2 = G_3 = 1$$
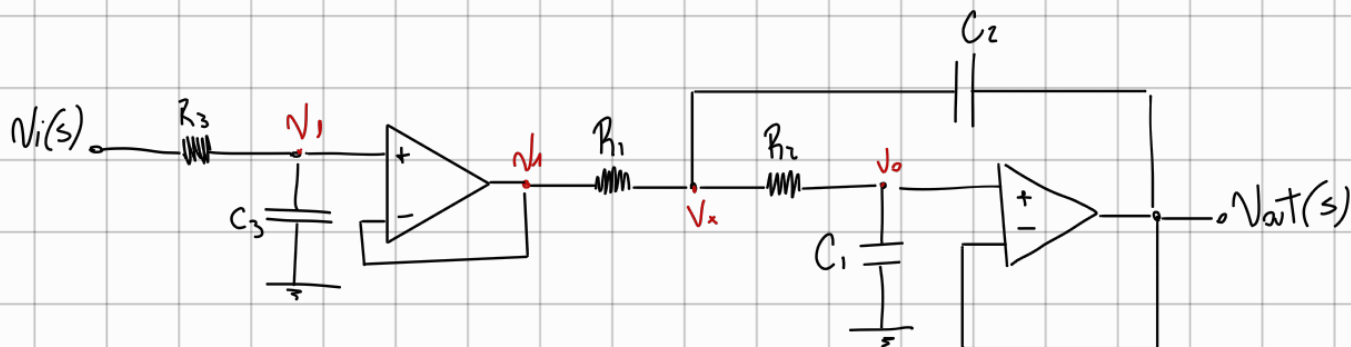
$$C_1 = \frac{1}{C_2 \cdot 6,46} \quad C_2 = \frac{2 G_1}{3,678} \quad C_3 = \frac{1}{(2,322) R_3}$$



Desnormalización para $D_0(d) = 200 \mu s$.

$$s = \frac{s'}{\frac{1}{200 \mu s}} \rightarrow s = \frac{s}{5000} // \text{ Mantengo } G_1 = G_2 = G_3 = 1 \text{ entonces:}$$

$$\text{Considerando la impedancia del cap. } Z_c = \frac{1}{sC} \rightarrow Z_c = \frac{1}{\frac{s}{5000}}$$

Desnormalizo

$$C'_3 = \frac{C_3}{5000} \quad C_3 = \frac{1}{2,312} = 0,43$$

$$C'_3 = 86 \mu F$$

$$C'_2 = \frac{C_2}{5000} \quad C_2 = \frac{2}{3,676} = 0,5437$$

$$C'_2 = 108,74 \mu F$$

$$C'_1 = \frac{C_1}{5000} \quad C_1 = \frac{1}{C_2(6,46)} = 0,2846$$

$$C'_1 = 56,92 \mu F$$